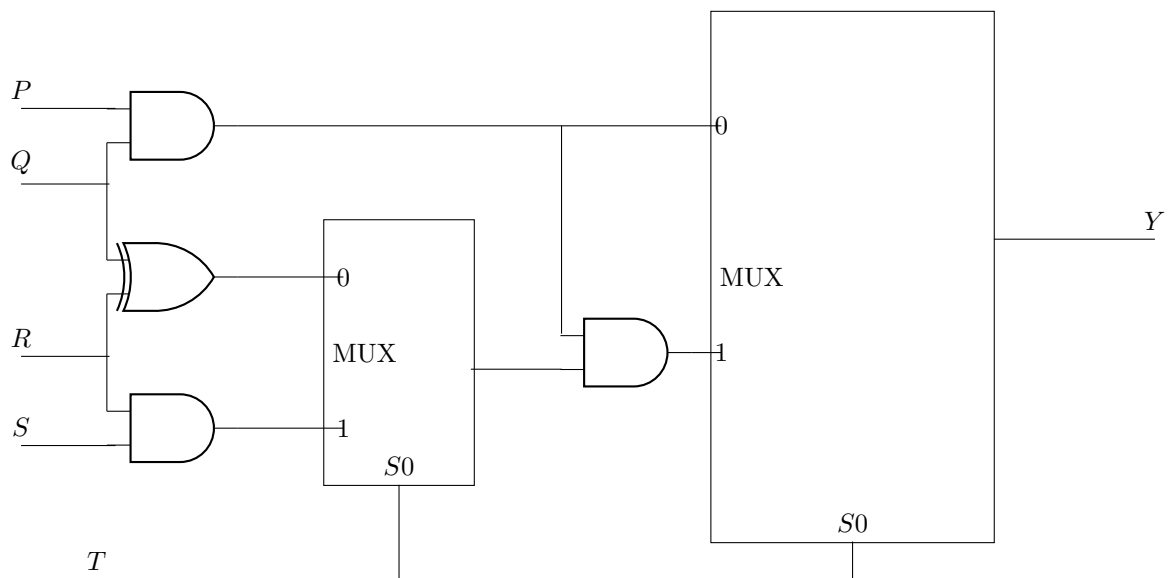


The below circuit is to be implemented using the 7447 IC.



## 1. Components

Table 1: Table1

COMPONENTS		
Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

## 2. Hardware

- Make Connections between the seven segment display in and the 7447 IC as shown in 2.

Table 2: Table2

7447 - Display							
7447	$\bar{a}$	$b$	$\bar{c}$	$d$	$\bar{e}$	$f$	$\bar{g}$
Display	a	b	c	d	e	f	g

- (b) Connect Vcc of the IC and COM of the display to 5V and the GND pins of the IC and display to the Ground of arduino.

### 3. Software

- (a) Now make the connections as per 3.

Table 3: Table3

7447 - Arduino				
7447	D	C	B	A
Arduino	5	4	3	2

- (b) In the truth table in 4, P,Q,R,S,T are the inputs and Y is the output.

Table 4: Table4

Truth Table					
0	x	x	x	1	0
x	0	x	x	1	0
x	x	0	x	x	0
x	x	x	0	x	0
x	x	1	1	0	1
1	1	1	1	x	1

- (c) Since, 7447 is a Seven Segment Display decoder, A represents the LSB and D represents the MSB. So giving the input to A displays either 0 or 1 on the Display.
- (d) Since, the output of the mux is either 0 or 1, this output of mux i.e., Y can be given as input to A of the 7447 IC so that the output of the mux can be observed directly on the display.
- (e) The boolean expression for the output (Y) of the second mux with the inputs (P,Q,R,S,T) will be simplified as 1

$$Y = T'PQ + PQRST. \quad (1)$$

- (f) The code below realizes the Boolean logic for A with y being the input to A.

```

//Declaring and initializing all variables as integers

int P=0,Q=0,R=0,S=0,T=0;
int A,B,C,D;

//function for A,B,C,D ins of 7447 IC

void disp(int D,int C,int B,int A){
digitalWrite(2,A);//LSB
digitalWrite(3,A);
digitalWrite(4,A);
digitalWrite(5,A);//MSB }

//the setup function runs once when you press reset or
power the board

void setup(){
pinMode(2,OUTPUT);
pinMode(3,OUTPUT);
pinMode(4,OUTPUT);
pinMode(5,OUTPUT);
}

//the loop function runs over and over again forever

void loop(){
A=(!T&&R&&S)||(P&&Q&&R&&S&&T);
B=0;
C=0;
D=0;
disp(D,C,B,A);
}

```

- (g) Execute the above code and compare the results of output theoretically and practically.